

33 The diagram shows a circuit.

Which resistor dissipates the least power?

