

34 A battery with internal resistance is connected by wires to an external resistor.

Which statement describes the electromotive force (e.m.f.) of the battery?

- A** It is the energy transferred per unit charge in driving charge through a connecting wire.
- B** It is the energy transferred per unit charge in driving charge through the complete circuit.
- C** It is the energy transferred per unit charge in driving charge through the external resistor.
- D** It is the energy transferred per unit charge in driving charge through the internal resistance.