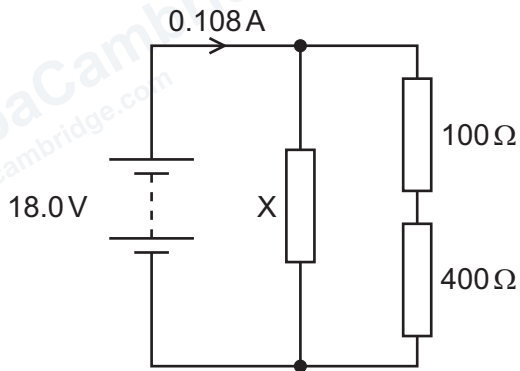


- 37** A battery of electromotive force (e.m.f.)  $18.0\text{ V}$  and negligible internal resistance is connected to a network of three fixed resistors as shown.



The current in the battery is  $0.108\text{ A}$ .

What is the resistance of resistor  $X$ ?

- A**  $125\ \Omega$       **B**  $167\ \Omega$       **C**  $250\ \Omega$       **D**  $500\ \Omega$