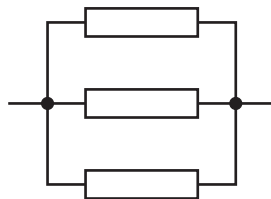



36 Three resistor networks, X, Y and Z, are formed from identical resistors as shown.



X



Y

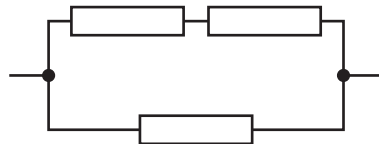

Z

What is the order of the networks from smallest total resistance to largest total resistance?

A $X \rightarrow Z \rightarrow Y$

B $Y \rightarrow X \rightarrow Z$

C $Y \rightarrow Z \rightarrow X$

D $Z \rightarrow Y \rightarrow X$