

35 Two resistors connected in parallel have a combined resistance of $8.0\ \Omega$.

One of the resistors has a resistance of $24\ \Omega$.

The two resistors are now connected in series.

What is their combined resistance?

A $20\ \Omega$

B $30\ \Omega$

C $32\ \Omega$

D $36\ \Omega$