

- 35** In the diagrams shown, the cells have negligible internal resistance and the wires have negligible resistance.

Which diagram demonstrates Kirchhoff's second law?

