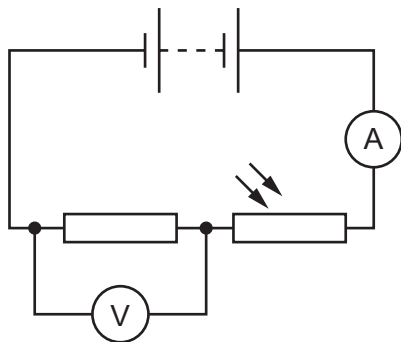


- 37 The diagram shows a resistor connected in series with a light-dependent resistor (LDR) and a battery.



The light intensity incident on the LDR increases.

What is the effect of this change on the voltmeter and ammeter readings?

	voltmeter reading	ammeter reading
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases