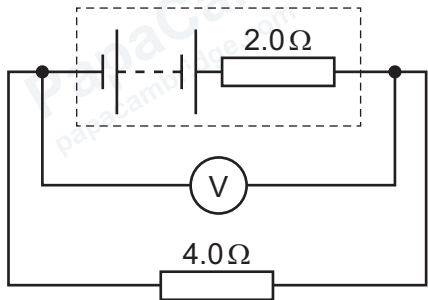


35 The diagram shows a circuit with a battery connected to a resistor with a resistance of $4.0\ \Omega$.



The battery has an internal resistance of $2.0\ \Omega$.

The voltmeter reads 12 V .

A second resistor of resistance $4.0\ \Omega$ is connected in parallel to the first resistor.

What is the new reading on the voltmeter?

A 6.0 V

B 9.0 V

C 12 V

D 24 V