

31 A resistor with a resistance R is connected to a cell.

The current in the resistor is I and the potential difference (p.d.) across the resistor is V .

Which equations can be used to calculate the power dissipated in the resistor?

1 $P = I^2 R$

2 $P = VI$

3 $P = \frac{V^2}{R}$

A 1, 2 or 3

B 1 or 2 only

C 1 only

D 2 only