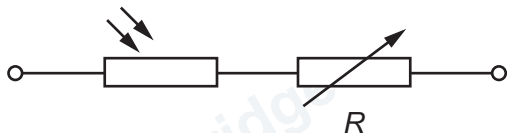


- 34** A variable resistor and a light-dependent resistor (LDR) are connected in series.



The resistance R of the variable resistor is adjusted so that, when light falls on the LDR, the combined resistance of the two resistors remains the same.

Which graph could represent the variation of R with the intensity of light that is incident on the LDR?

