

36 Which statement about the terminal potential difference (p.d.) of a power supply in a series circuit is correct?

- A** The difference between the electromotive force (e.m.f.) and the terminal p.d. of the power supply is equal to the total energy dissipated inside the power supply due to its internal resistance.
- B** The terminal p.d. of the power supply is equal to the e.m.f. when there is no current in the supply.
- C** The terminal p.d. of the power supply is the energy transferred in moving a unit charge around the complete circuit.
- D** The terminal p.d. of the power supply is always more than the e.m.f. due to the internal resistance of the supply.