

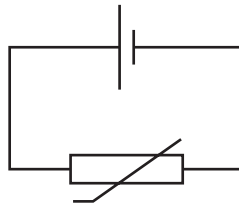
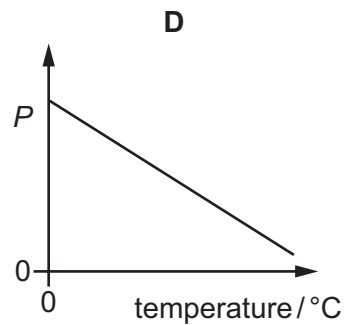
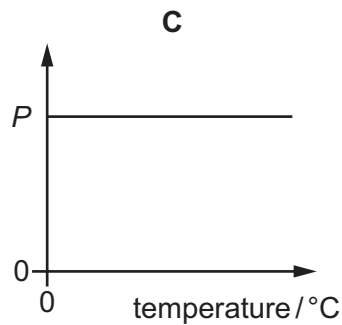


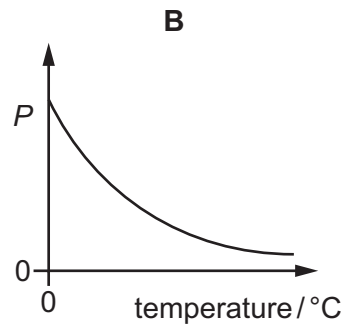- 32** A thermistor is connected to a cell with negligible internal resistance.



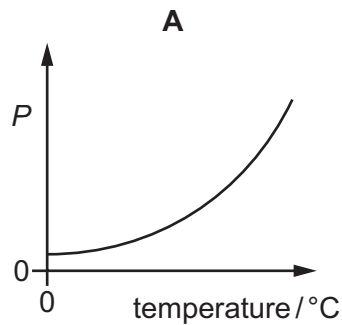Which graph shows the variation with temperature of power, P , dissipated in the thermistor?



- 33** A metal electrical conductor has a resistance of $5.6\text{ k}\Omega$. A potential difference (p.d.) of 9.0 V is