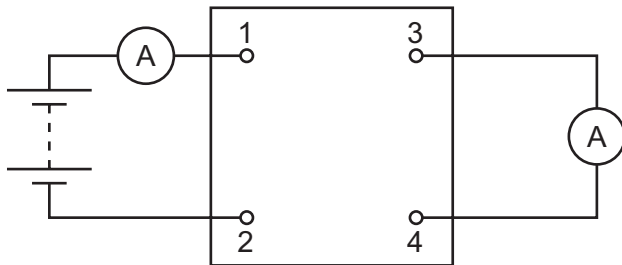



36 The diagram shows a four-terminal box connected to a battery and two ammeters.




The currents in the two ammeters are identical.

Which circuit, within the box, gives this result?


A

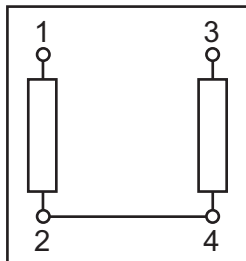

B

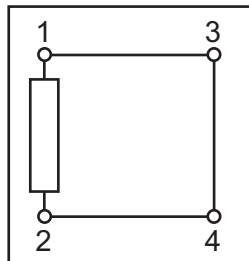

C

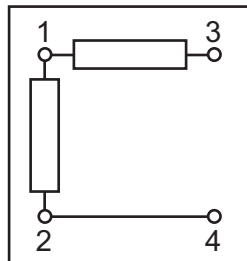

D

