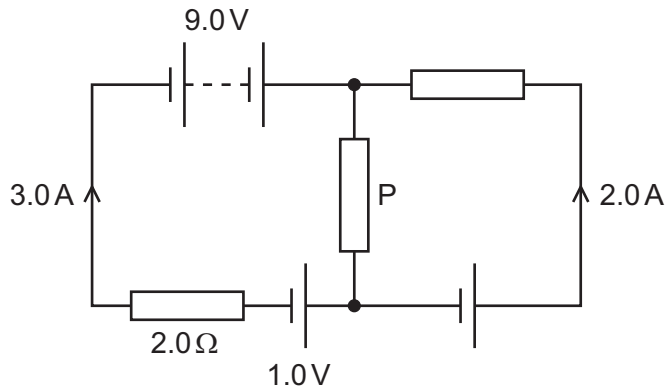


34 The diagram shows a circuit containing a battery and cells with negligible internal resistance.

Some values of current, electromotive force (e.m.f.) and resistance are shown.

One resistor is labelled P.



What is the resistance of resistor P?

A 0.40Ω

B 0.80Ω

C 2.0Ω

D 2.8Ω