

- 6 A battery of electromotive force (e.m.f.)  $6.0\text{ V}$  and negligible internal resistance is connected in series with a variable resistor and a uniform resistance wire XY, as shown in Fig. 6.1.

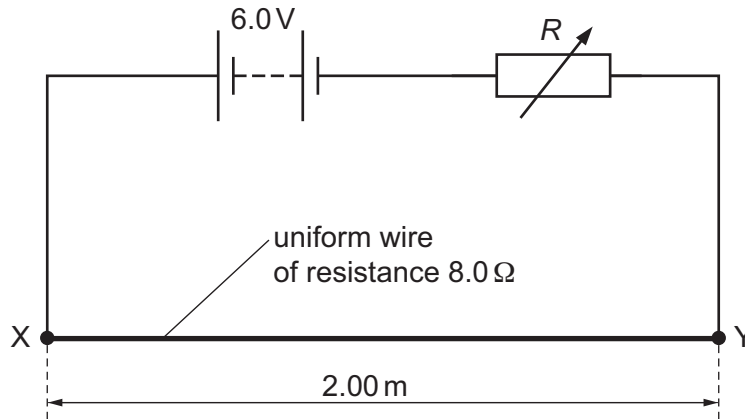


Fig. 6.1

Wire XY has length  $2.00\text{ m}$  and resistance  $8.0\ \Omega$ . The resistance  $R$  of the variable resistor is adjusted so that the potential difference across wire XY is  $2.4\text{ V}$ .

- (a) Determine  $R$ .

$R = \dots\dots\dots \Omega$  [2]

- (b) Explain why the potential difference  $V$  between any two points on wire XY is proportional to the distance  $L$  between those points.

.....  
 .....  
 .....  
 ..... [2]



(c) A cell of e.m.f.  $E$  and internal resistance  $r$  is connected to the circuit, as shown in Fig. 6.2.

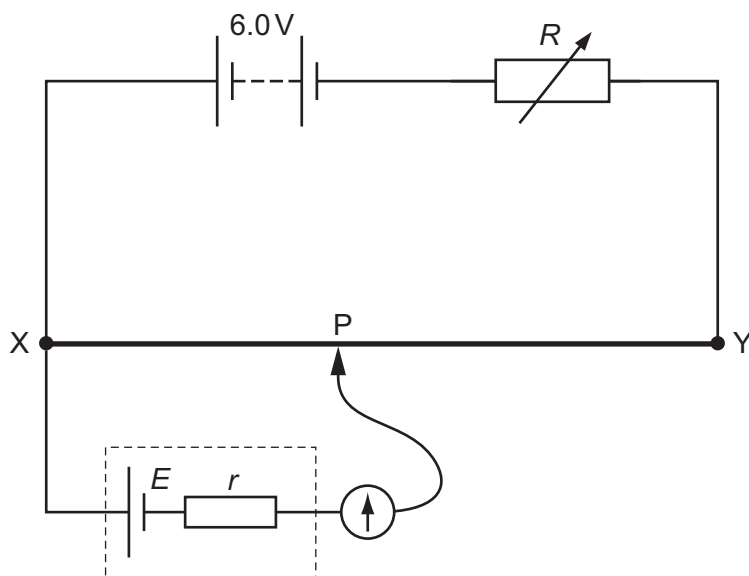


Fig. 6.2

Resistance  $R$  is unchanged.

The movable connection  $P$  is positioned on wire  $XY$  so that the galvanometer reading is zero. Distance  $XP$  is 1.24 m.

(i) Calculate  $E$ .

$$E = \dots\dots\dots \text{ V [2]}$$

(ii) The value of  $R$  is now decreased.

State and explain the change that must be made to the position of  $P$  on wire  $XY$  so that the galvanometer reads zero again.

.....  
 .....  
 .....  
 ..... [2]

[Total: 8]

