

28 The circuit diagrams show a cell connected to two diodes and a lamp in series.

In which circuit does the lamp light up?


A

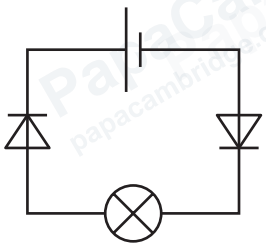


B

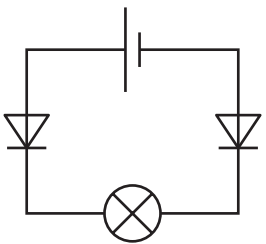

C

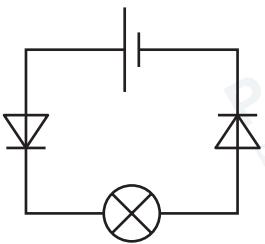

D

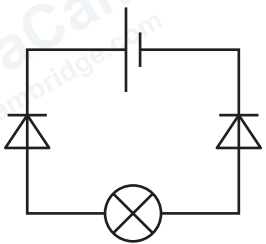

PapaCambridge
papacambridge.com