
29 The diagram shows a battery connected to two resistors, X and Y.

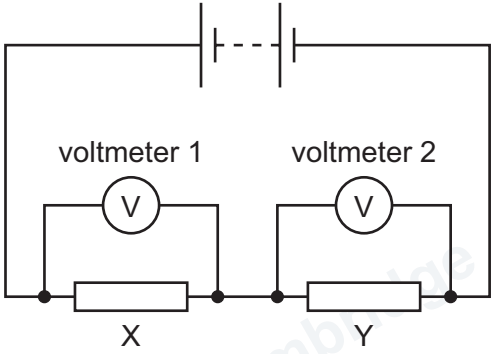Two voltmeters are connected into the circuit.



The reading on voltmeter 1 is greater than the reading on voltmeter 2.

Which row about the current in the two resistors and the resistance of the two resistors is correct?

	current	**size of resistors**
A	current is the same in both resistors	both resistors have the same resistance
B	current is the same in both resistors	resistance of X is greater than resistance of Y
C	current in X is greater than current in Y	both resistors have the same resistance
D	current in X is greater than current in Y	resistance of X is greater than resistance of Y