33 A transformer has a primary coil with 2000 turns and a secondary coil with 10 000 turns.

The transformer is 100% efficient.

V_p is the voltage across the primary coil.

V_s is the voltage across the secondary coil.

I_p is the current in the primary coil.

I_s is the current in the secondary coil.

Which statement about this transformer is correct?

A $V_s = V_p \times 5$ and $I_s = I_p \times 5$

B $V_s = V_p \times 5$ and $I_s = I_p \times 0.2$

C $V_s = V_p \times 0.2$ and $I_s = I_p \times 5$

D $V_s = V_p \times 0.2$ and $I_s = I_p \times 0.2$

PapaCambridge
papacambridge.com