26 Which statement about a voltmeter is correct?

A It has a scale which is marked in amperes (A).

B It must be connected in series in a circuit.

C It measures potential difference (p.d.).

D It must have three terminals.