

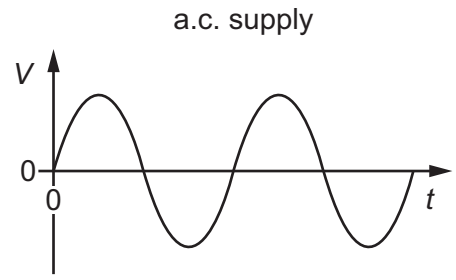
29 An alternating (a.c.) supply is connected to a diode and a resistor in series.



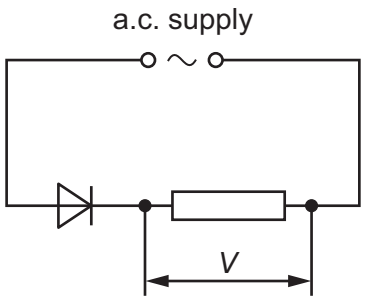


Which graph shows how the potential difference *V* across the resistor varies with time *t*?


A

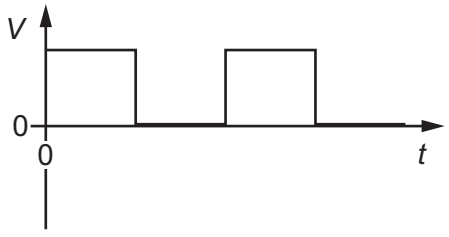

B

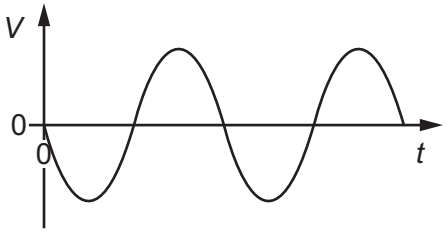

C

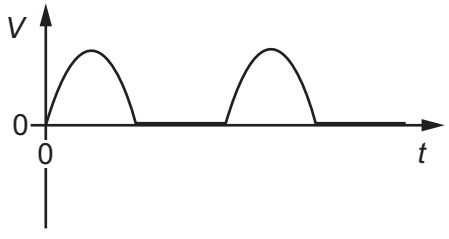

D

