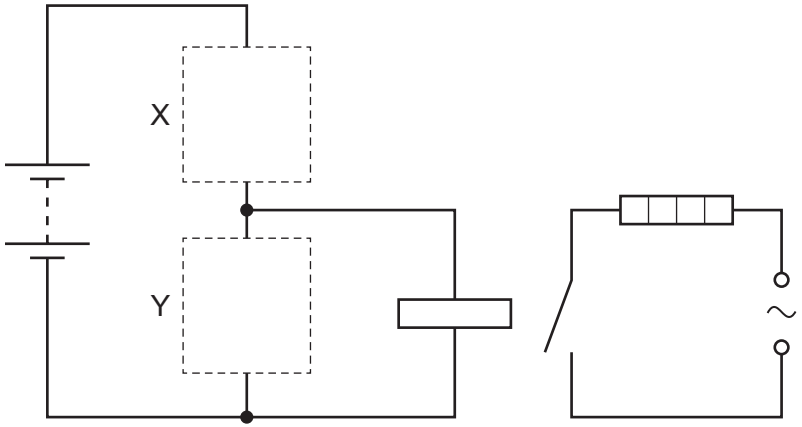
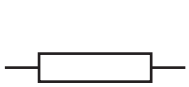
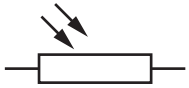
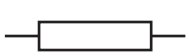
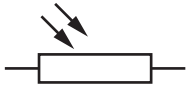
30 The diagram shows a circuit used to switch on a heater when the temperature drops below a certain value.



Which row shows the components that should be connected at X and at Y?

	X	Y
A		
B		
C		
D		