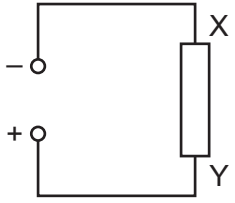
25 A power source is connected to a resistor XY.



In which directions are the conventional current and the flow of free electrons through the resistor?

	conventional current	free electron flow
A	X to Y	X to Y
B	X to Y	Y to X
C	Y to X	X to Y
D	Y to X	Y to X