
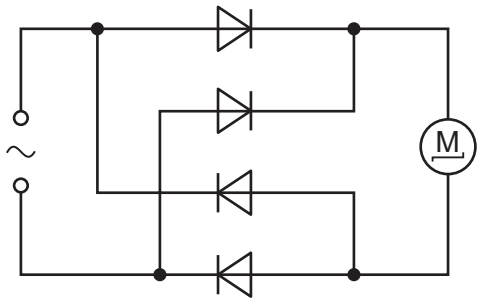
29 The circuit diagram shows a circuit used to run a d.c. motor from an a.c. supply.




Which graph shows the current in the motor?


A

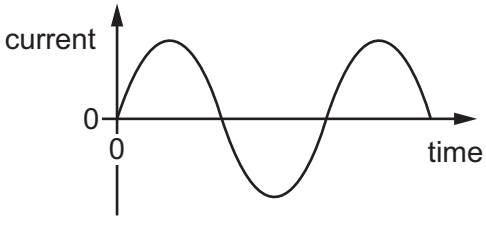

B

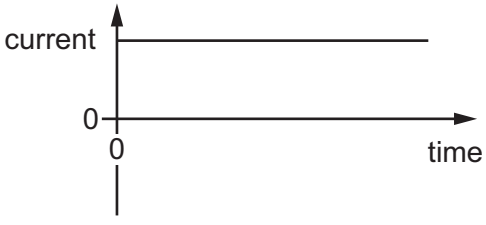

C

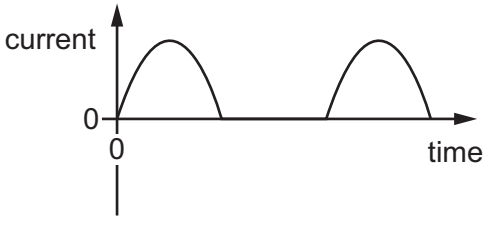

D

