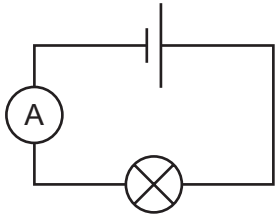
25 The diagram shows an electric circuit.



In which direction do free electrons flow around this circuit and what quantity does the ammeter measure?

	direction of electron flow	quantity measured by the ammeter
A	anticlockwise	charge passing each point in the circuit per unit time
B	anticlockwise	total charge passing through the ammeter
C	clockwise	charge passing each point in the circuit per unit time
D	clockwise	total charge passing through the ammeter