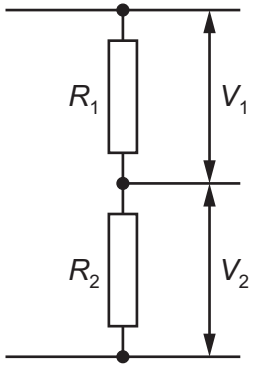
29 Two resistors, with resistances R_1 and R_2, are used as a potential divider.



What is the relationship between R_1, R_2 and potential differences V_1 and V_2?

A $R_1 \times R_2 = V_1 \times V_2$

B $R_1 \times V_1 = R_2 \times V_2$

C $\dfrac{R_1}{R_2} = V_1 \times V_2$

D $\dfrac{R_1}{R_2} = \dfrac{V_1}{V_2}$