
**25** The diagram shows a transformer.

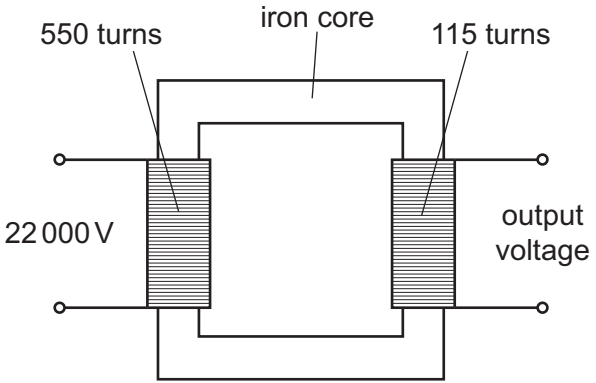


What is the output voltage?

**A** 0.35 V **B** 2.9 V **C** 4600 V **D** 105 000 V