28 A student has two resistors.

One resistor has a resistance of 2.0 Ω and the other has a resistance of 40 kΩ.

Which statement is correct?

A When connected in parallel, the combined resistance is 1.9 Ω.

B When connected in parallel, the combined resistance is 2.0 Ω.

C When connected in series, the combined resistance is 1.9 Ω.

D When connected in series, the combined resistance is 42 Ω.