

29 In which circuit do both lamps light?


A

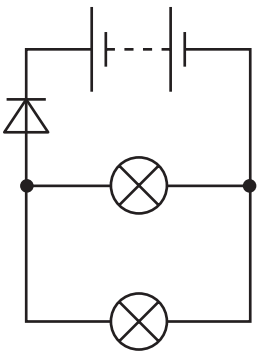

B

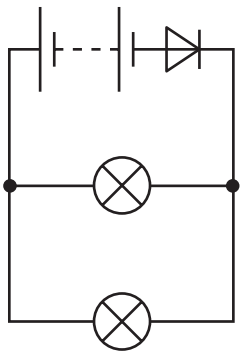

C

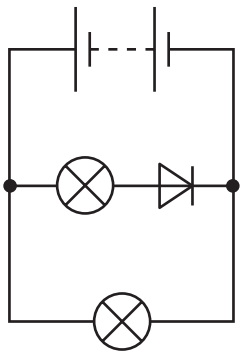

D

