26 A resistor of resistance R is connected to a battery of electromotive force (e.m.f.) V.

There is a current I in the resistor.

Power P is dissipated by the resistor.

In time t, the energy transferred is E.

Which expression is correct?

A $E = IVt$ **B** $E = PIt$ **C** $P = VIR$ **D** $P = \frac{V}{R}$