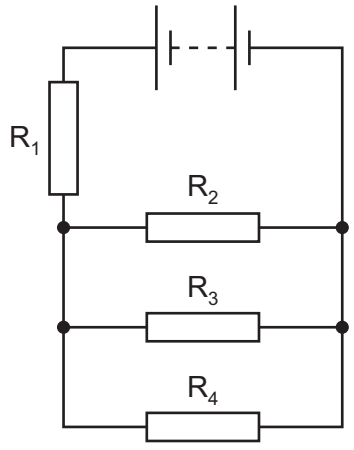
**28** Four identical resistors are connected to a battery as shown. Each resistor has a value of 120 Ω.




Resistor $R_4$ is removed.

Which effect does removing this resistor have on the effective resistance of the circuit?

**A** The effective resistance does **not** change.

**B** The effective resistance decreases by 20 Ω.

**C** The effective resistance increases by 20 Ω.

**D** The effective resistance decreases by 120 Ω.