
**29** The resistors in the circuit shown are identical.

The reading on voltmeter $V_2$ is 1.5 V.

The reading on ammeter $A_2$ is 0.50 A.

The reading on ammeter $A_3$ is 0.25 A.

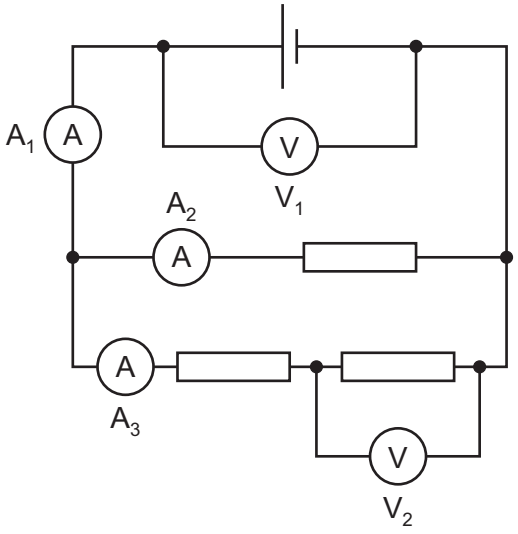


What are the readings on ammeter $A_1$ and voltmeter $V_1$?

| | ammeter $A_1$ / A | voltmeter $V_1$ / V |
|---|---|---|
| **A** | 0.25 | 1.5 |
| **B** | 0.25 | 3.0 |
| **C** | 0.75 | 1.5 |
| **D** | 0.75 | 3.0 |