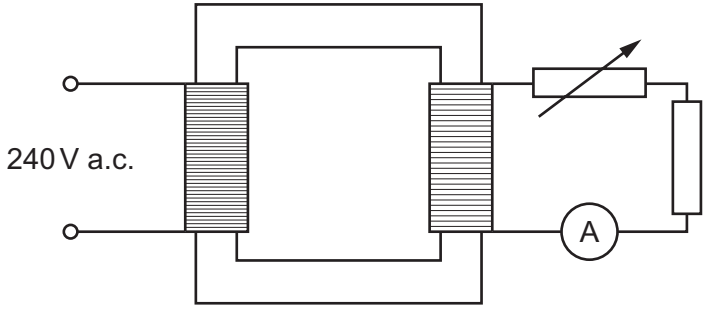
31 A fixed resistor is connected to the secondary coil of a step-down transformer. The transformer is 100% efficient.



The variable resistor is adjusted so that the current in the fixed resistor decreases by 0.25 A.

What is the change to the current in the primary circuit?

A It decreases by 0.25 A.

B It decreases by less than 0.25 A.

C It decreases by more than 0.25 A.

D There is no change.