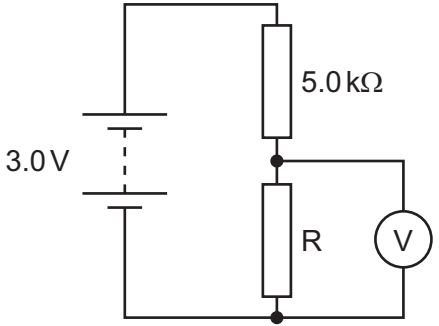
29 The diagram shows two resistors used as a potential divider.



The reading on the voltmeter is 1.8 V.

What is the resistance of the resistor R?

A 3.0 kΩ **B** 3.3 kΩ **C** 7.5 kΩ **D** 13 kΩ