32 A 24 V power supply and a 100% efficient transformer are used to light a 6.0 V, 12 W lamp.

What is the current in the power supply?

A 0.50 A **B** 2.0 A **C** 3.0 A **D** 8.0 A