

28 Which circuit shows the directions of the conventional current I and the flow of electrons?


A

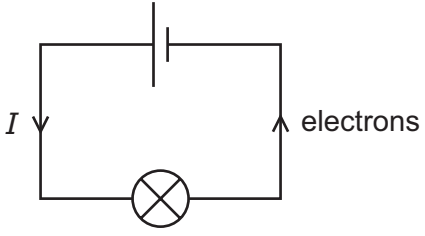

B

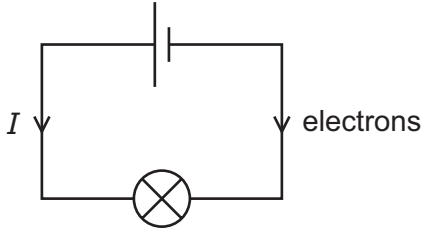

C

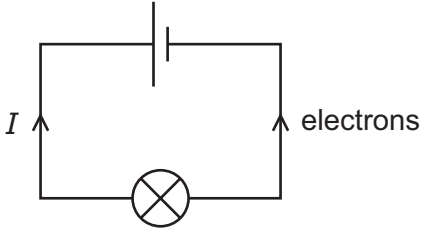

D

