29 A cell has an electromotive force (e.m.f.) of 1.5 V.

How much energy is transferred by the cell when it drives 6.0 C of charge round a complete circuit?

A 4.0 J **B** 4.0 W **C** 9.0 J **D** 9.0 W