
31 The diagram shows two circuits.

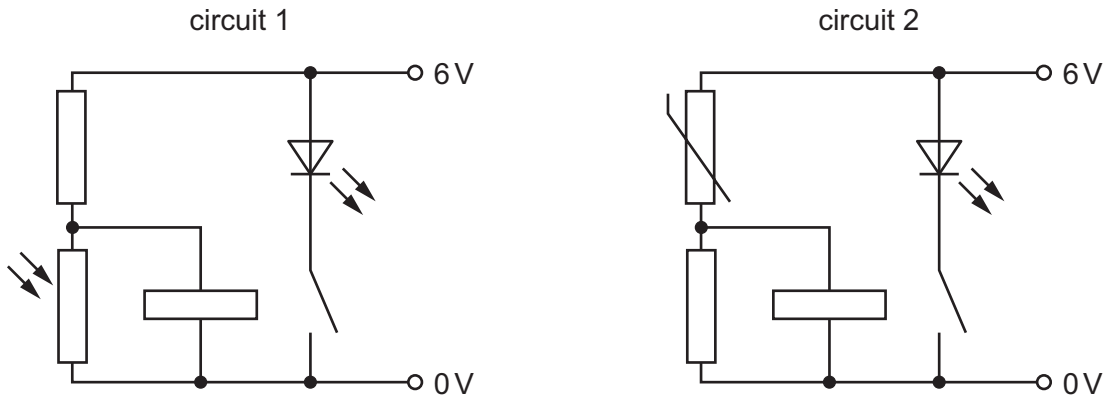Each relay is normally open when there is no current in the coil.



Which environmental conditions will cause the light-emitting diodes in circuit 1 and circuit 2 both to emit light?

	temperature	light intensity
A	high	high
B	high	low
C	low	high
D	low	low