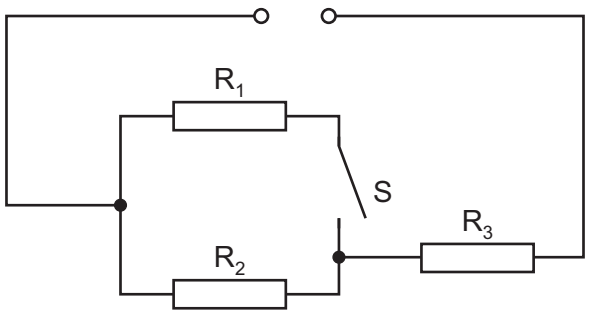
**27** The diagram shows three 20 Ω resistors, $R_1$, $R_2$ and $R_3$, and a switch S connected to a d.c. power supply.




Switch S is open.

The potential difference (p.d.) across $R_3$ is 9.0 V.

What is the p.d. across $R_3$ when switch S is closed?

**A** 3.0 V **B** 6.0 V **C** 12 V **D** 27 V