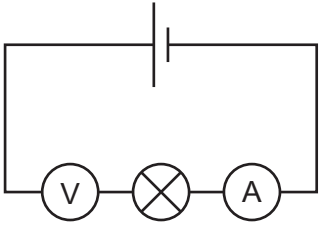
27 A student is trying to determine the resistance of a lamp. He sets up the **incorrect** circuit shown.



Which change would allow him to take the measurements needed to calculate the resistance of the lamp?

A Disconnect the ammeter and move it to the left of the lamp.

B Swap the positions of the ammeter and the voltmeter in the circuit.

C Disconnect the ammeter and connect it in parallel with the lamp.

D Disconnect the voltmeter and connect it in parallel with the lamp.