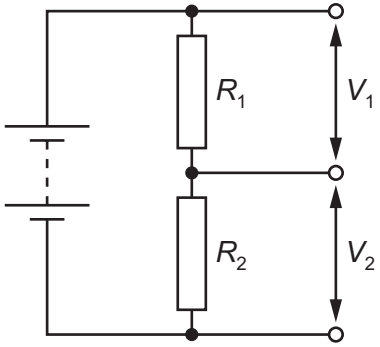
29 The diagram shows the circuit for a potential divider.



Which equation is used to calculate V_1?

A $V_1 = \dfrac{R_1}{V_2 \times (R_1 + R_2)}$

B $V_1 = \dfrac{V_2 \times R_1}{R_2}$

C $V_1 = \dfrac{V_2 \times R_1}{R_1 + R_2}$

D $V_1 = \dfrac{R_1}{V_2 \times R_2}$