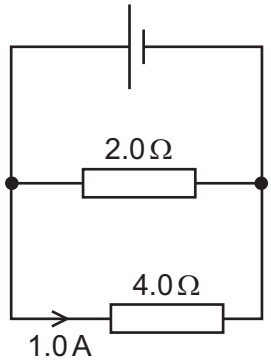
31 A cell is connected to a parallel combination of a 2.0 Ω resistor and a 4.0 Ω resistor. The current in the 4.0 Ω resistor is 1.0 A.



What is the current in the cell?

A 1.0 A **B** 1.5 A **C** 2.0 A **D** 3.0 A