33 The primary voltage supplied to a transformer is 3.0 V. The secondary voltage is 5.0 V and the secondary current is 2.0 A. The transformer is 100% efficient.

What is the primary current in the transformer?

A 1.2 A **B** 2.0 A **C** 3.3 A **D** 7.5 A