26 A circuit contains a cell with an electromotive force (e.m.f.) of 2.0 V. The current in the circuit is 2.0 A.

How much energy is transferred by the cell in 2.0 minutes?

A 2.0 J **B** 4.0 J **C** 8.0 J **D** 480 J