28 Four lamps and four switches are connected to a power supply, as shown.

When all the switches are closed, all the lamps are lit.

When one of the switches is then opened, only **one** lamp goes out.

Which switch is opened?

