

28 Which circuit contains a diode connected in series with a fixed resistor?


A

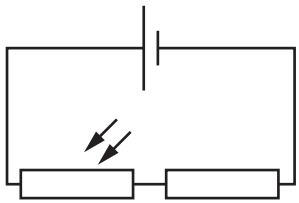

B

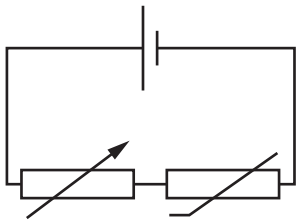

C

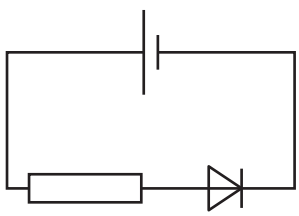

D

