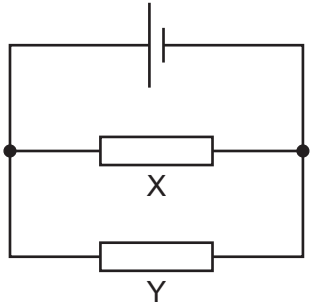
29 In the circuit shown, resistor X has twice the resistance of resistor Y.



Which statement about the circuit is correct?

A The current in the cell is greater than the current in X.

B The current in X is greater than the current in Y.

C The potential difference (p.d.) across the cell is greater than the p.d. across X.

D The p.d. across X is greater than the p.d. across Y.