30 A 4 Ω resistor and an 8 Ω resistor are connected in series with a power supply.

A voltmeter connected across the 8 Ω resistor reads 36 V.

What is the voltmeter reading when it is connected across the 4 Ω resistor?

A 12 V **B** 18 V **C** 72 V **D** 108 V