33 Two transformers, P and Q, each have 2000 turns on their primary coils and 1000 turns on their secondary coils. Both transformers are 100% efficient.

The secondary of transformer P is connected to the primary of transformer Q.

Q provides a motor with a current of 0.2 A.

What is the current being supplied to the primary of transformer P?

A 0.8 A **B** 0.4 A **C** 0.1 A **D** 0.05 A