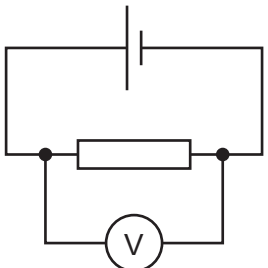
26 In the circuit shown, the voltmeter reads 2.0 V. A charge of 5.0 C passes through the resistor in a certain time.



How much energy is supplied to the resistor in this time?

A 0.40 J **B** 2.5 J **C** 10 J **D** 20 J