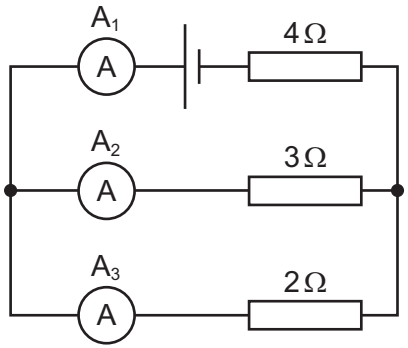
28 The diagram shows an electrical circuit.



Which statement is correct?

A The current reading on ammeter A_1 is the highest.

B The current reading on ammeter A_2 is the highest.

C The current reading on ammeter A_3 is the highest.

D The current readings on all three ammeters A_1, A_2 and A_3 are the same.